

# Application Note 107

## A Bias Sequencing Circuit for Amplifiers Requiring a Negative Gate Voltage

### Introduction

When using depletion mode devices in amplifiers, both a positive and a negative voltage supply are required for operation, which doesn't normally present a problem so long as the negative voltage (gate control) is applied first. However, if the positive voltage (drain side) is applied first, the results can be catastrophic—device destruction being the most common outcome. Such destruction can also happen if the negative voltage is turned off first. To solve this problem, Custom MMIC has developed a sequencer circuit to ensure that the voltages are turned both on and off in the correct order, so that the device is not damaged.

### Circuit Operation

A simplified block diagram of Custom MMIC's sequence circuit is shown in Figure 1. Here, U1 and U4 are voltage regulators, U2 is a negative voltage generator, and U3 is a comparator to control the timing of the circuit. The input voltage,  $V_1$ , powers both U1 and U4. The regulated drain voltage,  $V_4$ , is provided directly from U4 to the drain of the amplifier, but only when it receives an enable signal from U3. U1 produces a regulated voltage,  $V_2$ , which can provide a positive  $V_{gg2}$  gate voltage to the DUT (if needed). Voltage  $V_2$  also powers the negative voltage generator U2 and the comparator U3. The output of U2 is applied to the DUT as  $V_{gg1}$ . As for timing, the comparator is designed such that once  $V_2$  is within 5% of Ref (a preset value), it will send the enable signal to U4. Then, and only then, is  $V_4$  applied to the DUT. Since  $V_4$  will not be enabled until it has received the signal from U3, we are guaranteed that  $V_{gg1}$ , the negative gate voltage, is applied before the positive drain voltage.

A functional schematic of the sequencer circuit is shown in Figure 2, while a PCB layout is provided in Figure 3. Here, we note the output voltages  $V_{gg1}$ ,  $V_{gg2}$ , and  $V_4$  can be set through external resistors. For example,  $V_{gg1}$  is controlled by resistors  $R_5$  and  $R_6$ , whereas  $V_{gg2}$  is controlled by  $R_1$  and  $R_2$ , and  $V_4$  is set by  $R_9$  and  $R_{10}$ . A table of resistor values for different Custom MMIC parts is provided at the end of this note in Table 1.

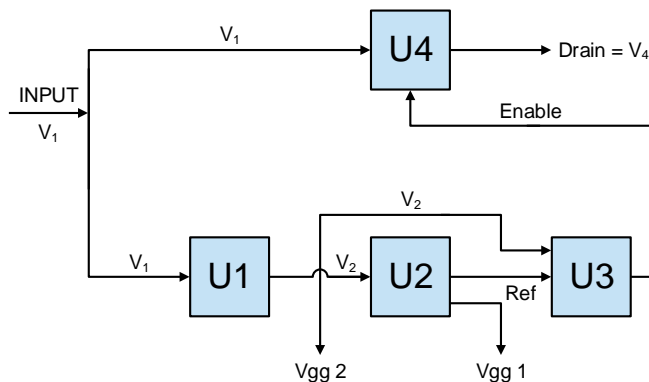


Figure 1. Block Diagram Of The Sequencer Circuit.

## Full Schematic

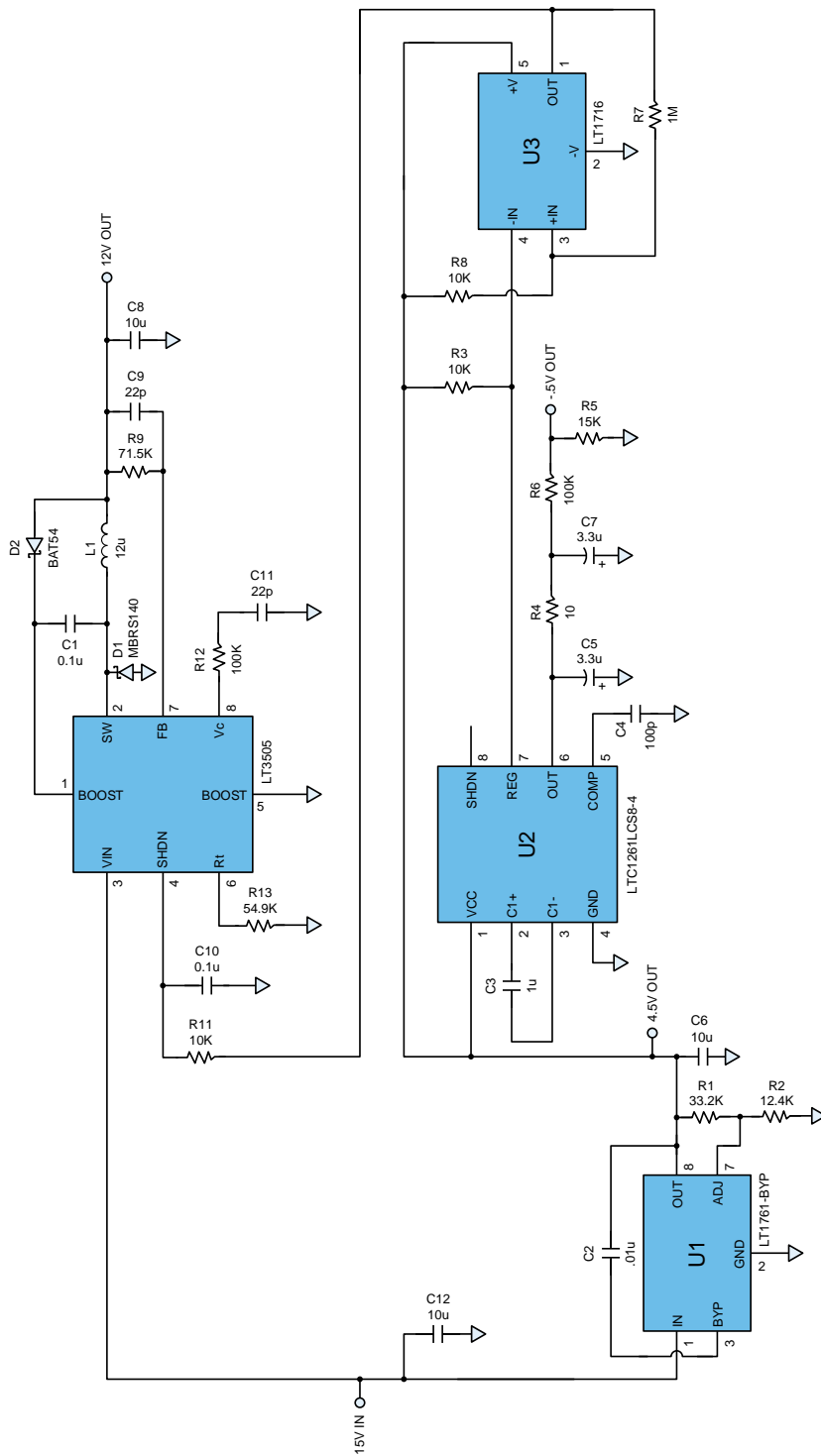


Figure 2. Schematic Of The Sequencer Circuit.

## Assembly Drawing

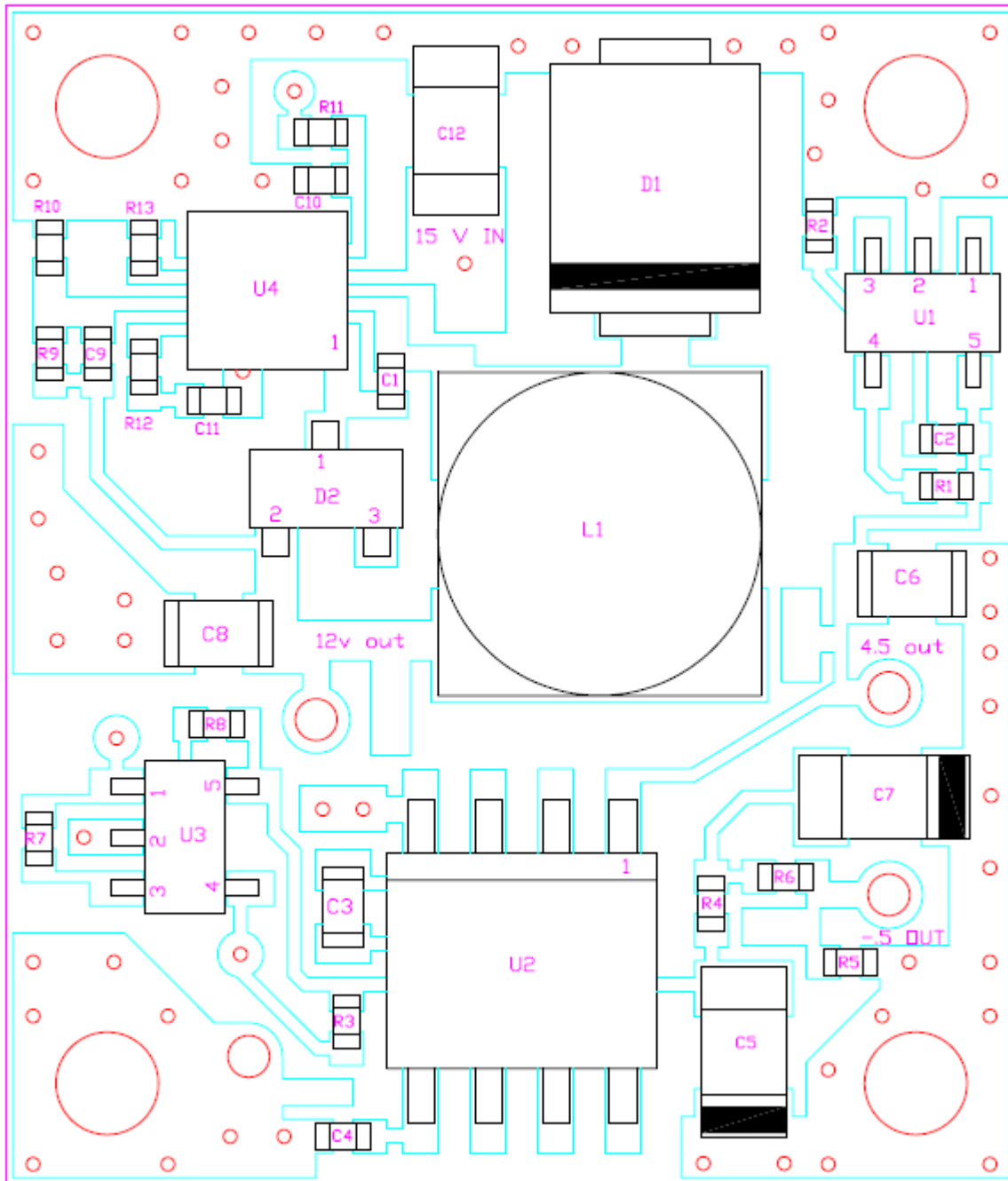


Figure 3. PCB Layout Of The Sequencer Circuit.

## Sequencer Testing

To demonstrate performance of the circuit, we assembled the sequencer circuit described in Figures 2 and 3, and chose resistor values using the equations provided in Table 1 such that output (drain) voltage  $V_4$  was 12 V and the gate voltage  $V_{gg1}$  was  $-0.58$  V. In Figure 4, we present a timing diagram the drain voltage and  $V_{gg1}$  as the external supply voltage,  $V_1$ , is cycled on and then off. We note that on the rising edge (near 0.3 s),  $V_{gg1}$  reaches its negative value before the drain voltage  $V_4$  is turned on, as intended. At the falling edge near 1.2 seconds, the external supply voltage  $V_1$  is turned off, and it is clear that the drain voltage  $V_4$  turns off before  $V_{gg1}$  turns off. We experimented with different levels of drain ( $V_4$ ) and gate ( $V_{gg1}$ ) levels, and in all cases the results were identical in terms of sequencing.

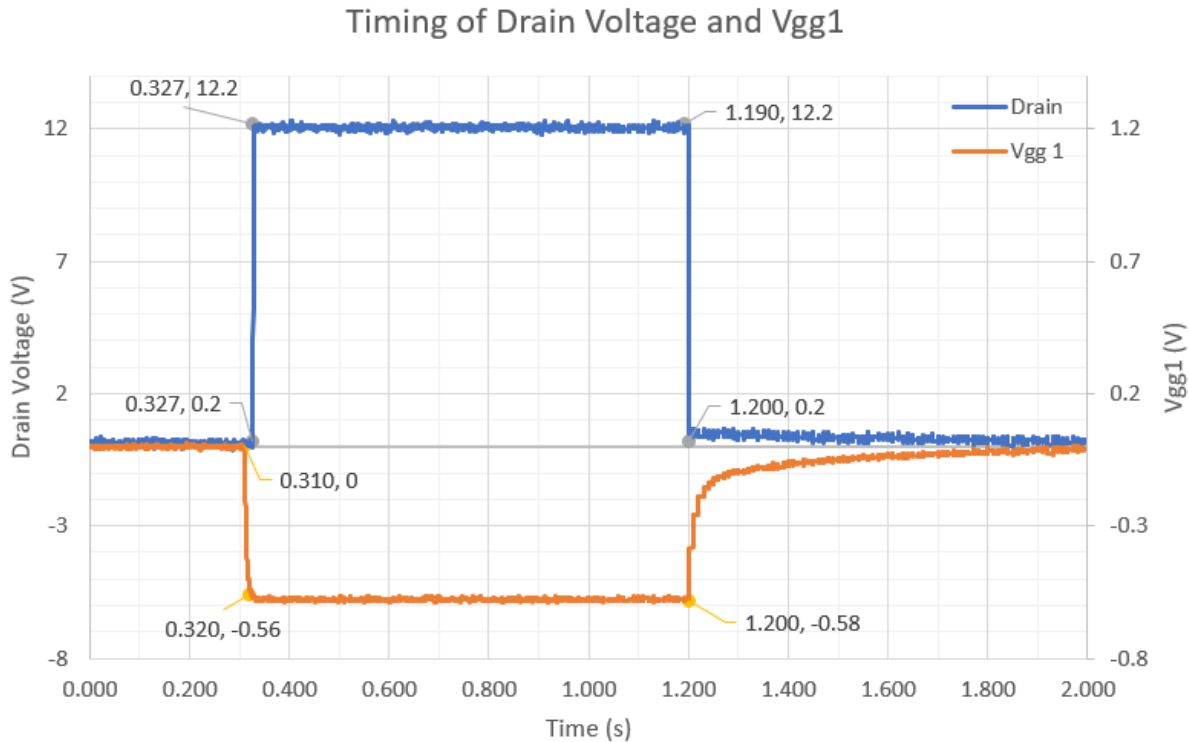


Figure 4. Timing Diagram For Drain Voltage  $V_4$  And Gate Voltage  $V_{gg1}$ .

## Sequencer Applied to CMD201P5

Our next step was to use the sequencer to power a Custom MMIC amplifier. For this demonstration we chose the CMD201P5, which requires the following voltages for operation:  $V_4 = 10\text{ V}$ ,  $V_{gg1} = -0.5\text{ V}$ , and  $V_{gg2} = +5\text{ V}$ . Using the equations shown at the end of Table 1, we determined the necessary resistor values for R1, R2, R5, R6, R9, and R10 to generate these voltages. We then tested the sequencer without the CMD201P5 applied to make sure the timing and levels were correct. We next used the sequencer board to power up a CMD201P5 and then we measured the amplifier's S-parameters on a network analyzer. In Figure 5, we present the results of this measurement, which shows normal operation for the CMD201P5. Indeed, there is no significant difference between these results and those obtained from manually biasing the CMD201P5 with separate dedicated supplies that were turned on in the proper sequence. Therefore, these results illustrate that the bias sequencing circuit both assures that all of the voltages are applied in the proper sequence and that it does not negatively impact the RF performance of the amplifier.

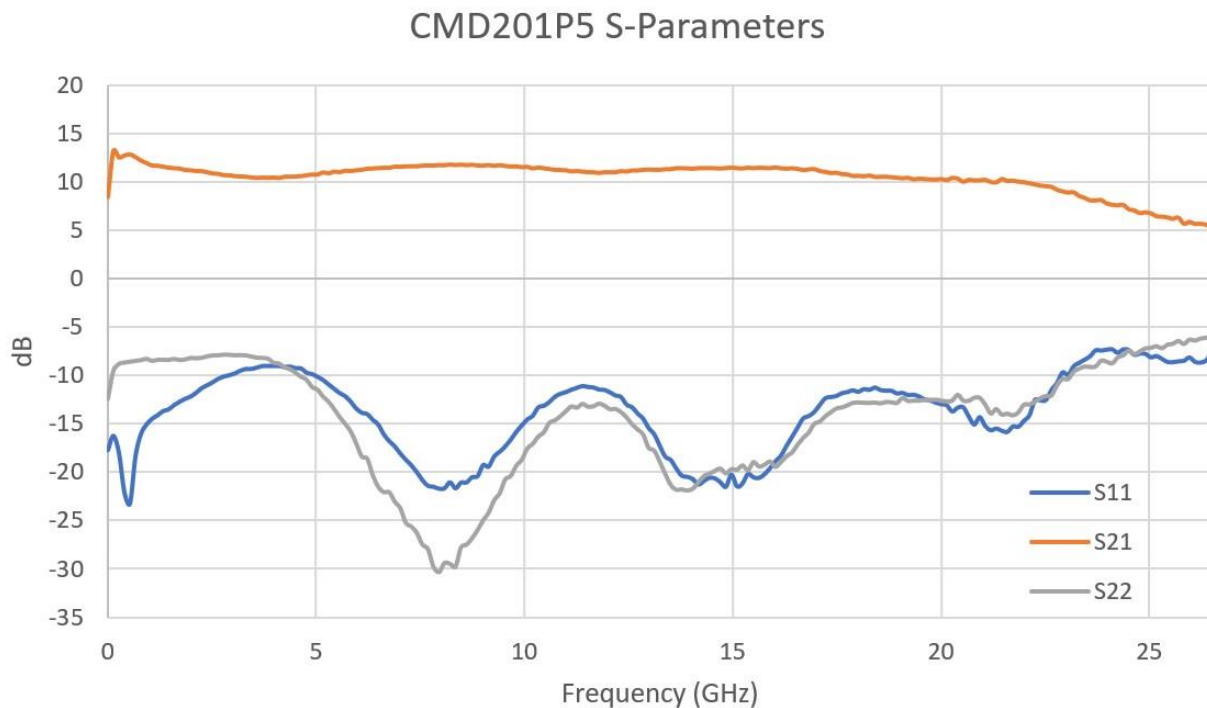


Figure 5. Measured S-Parameters Of CMD201P5 Using Sequencer Bias Circuit.

## Table of Resistor Values

In Table 1 below, we present the resistor values (1% tolerance required) needed to produce the voltages listed for each Custom MMIC depletion mode amplifier. The equations to calculate these values are also stated below. Please note that all voltages listed are typical values for each part and may vary in practice.

PART CMD	R1 (Ω)	R2 (Ω)	R5 (Ω)	R6 (Ω)	R9 (Ω)	R10 (Ω)	DRAIN V <sub>4</sub>	V <sub>gg1</sub> (V)	V <sub>gg2</sub> (V)
192/C5	100k	33.2k	Open*	1.74k	93.1k	10k	8	-1	N/A
201/P5	100k	32.4k	15.8k	100k	59k	4.99k	10	-0.55	5
218/C4	100k	33.2k	57.6k	42.2k	59k	4.99k	10	-2.3	N/A
219/C4	100k	33.2k	57.6k	42.2k	59k	4.99k	10	-2.3	N/A
240/P4	100k	33.2k	10k	56.2k	53.6k	10k	5	-0.6	N/A
241/P4	100k	33.2k	10k	51.1k	53.6k	10k	5	-0.65	N/A
242	100k	33.2k	10k	115k	93.1k	10k	8	-0.32	N/A
244	100k	33.2k	Open*	1.87k	93.1k	10k	8	-1	N/A
249	100k	33.2k	10k	31k	59k	4.99k	10	-0.95	N/A
276C4	100k	33.2k	57.6k	42.2k	59k	4.99k	10	-1.5	N/A
277C4	100k	33.2k	10k	10k	59k	4.99k	10	-2	N/A
278/C4	100k	33.2k	11.8k	13.7k	59k	4.99k	10	-1.85	N/A
291	100k	33.2k	10k	69.8k	53.6k	10k	5	-0.5	N/A
292	100k	53.6k	10k	71.5k	59k	4.99k	10	-0.5	3.5
293	100k	33.2k	10k	78.7k	53.6k	10k	5	-0.45	N/A
304	100k	33.2k	10k	88.7k	28.7k	10k	3	-0.4	N/A

Table 1. Summary of 1% resistor values required for the correct bias of each Custom MMIC part.

$$V_{drain} = 0.75 \left( \frac{R9}{R10} + 1 \right)$$

$$V_{gg1} = -4 \left( \frac{R5}{R5 + R6} \right)$$

$$V_{gg2} = 1.22 \left( 1 + \frac{R1}{R2} \right) + (30 \cdot 10^{-9}(R1))$$

\* The CMD192/C5 and CMD244 both include shunt resistors which need to be accounted for when calculating the value of R6. For the CMD192/C5 the effective resistance of R5 is 588 Ω and for the CMD244 it is 633 Ω.

## Acknowledgements

Custom MMIC would like to acknowledge the following for their contributions to this application note: Sarah McKinley, a 2018 Custom MMIC Women in Engineering Scholarship winner who is currently studying mechanical engineering at Clarkson University; and John Blount and Brian Salchert, 2019 summer high school interns.

## Additional Information

For information on ESD, Soldering Profiles, Packaging Standards, Handling and Assembly, please contact Qorvo for general guidelines.

## Contact Information

For the latest specifications, additional product information, worldwide sales and distribution locations:

**Web:** [www.qorvo.com](http://www.qorvo.com)

**Tel:** +1 833-641-3811

**Email:** [customer.support@qorvo.com](mailto:customer.support@qorvo.com)

## Important Notice

The information contained herein is believed to be reliable; however, Qorvo makes no warranties regarding the information contained herein and assumes no responsibility or liability whatsoever for the use of the information contained herein. All information contained herein is subject to change without notice. Customers should obtain and verify the latest relevant information before placing orders for Qorvo products. The information contained herein or any use of such information does not grant, explicitly or implicitly, to any party any patent rights, licenses, or any other intellectual property rights, whether with regard to such information itself or anything described by such information. **THIS INFORMATION DOES NOT CONSTITUTE A WARRANTY WITH RESPECT TO THE PRODUCTS DESCRIBED HEREIN, AND QORVO HEREBY DISCLAIMS ANY AND ALL WARRANTIES WITH RESPECT TO SUCH PRODUCTS WHETHER EXPRESS OR IMPLIED BY LAW, COURSE OF DEALING, COURSE OF PERFORMANCE, USAGE OF TRADE OR OTHERWISE, INCLUDING THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE.**

Without limiting the generality of the foregoing, Qorvo products are not warranted or authorized for use as critical components in medical, life-saving, or life-sustaining applications, or other applications where a failure would reasonably be expected to cause severe personal injury or death.

Copyright 2020 © Qorvo, Inc. | Qorvo is a registered trademark of Qorvo, Inc.